



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**BTECH**  
**(SEM VI) THEORY EXAMINATION 2021-22**  
**ANALOG SIGNAL PROCESSING**

**Time: 3 Hours****Total Marks: 100****Note:** Attempt all Sections. If you require any missing data, then choose suitably.**SECTION A****1. Attempt all questions in brief.****2\*10 = 20**

Q. No	Questions	CO
(a)	Enlist any two comparisons between Analog and Digital Signal Processing.	1
(b)	Enlist the significance about the term Sallen -Key biquad.	1
(c)	Define term Feedback with suitable example.	2
(d)	Enlist the widely used analog filters.	2
(e)	Explain signal rectification.	3
(f)	What do you mean by peak and valley?	3
(g)	Explain the term grounded inductor.	4
(h)	Define transconductance.	4
(i)	Define voltage limiter circuit.	5
(j)	Define gyrator with example.	5

**SECTION B****2. Attempt any three of the following:****10\*3 = 30**

Q. No	Questions	CO
(a)	Discuss the differentiation and addition linear analog function with suitable example	1
(b)	Discuss the Comparatively analysis between Maximally Flat and Equal Ripple responses.	2
(c)	Enlist the outcome for Equalization of First order and second order modules with suitable example	3
(d)	Explain Gorski-Popiel's Embedding technique with suitable example.	4
(e)	Explain the following terms: (I) Amplifiers (II) Gyrator (III) Integrator (IV) Registers	5



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**BTECH**  
**(SEM VI) THEORY EXAMINATION 2021-22**  
**ANALOG SIGNAL PROCESSING**

**SECTION C**

3. Attempt any *one* part of the following: **10\*1 = 10**

Q. No	Questions	CO
(a)	Describe the working of op-amp as an amplitude demodulator	1
(b)	Describe the working of Current Feedback Amplifier with suitable example.	1

4. Attempt any *one* part of the following: **10 \*1 = 10**

Q. No	Questions	CO
(a)	Draw and explain the first order Butterworth active low pass filter using Op-amp with its associated circuit diagram and transfer function.	2
(b)	Explain the Practical Differentiator circuit using Op-amp with its associated frequency response.	2

5. Attempt any *one* part of the following: **10\*1 = 10**

Q. No	Questions	CO
(a)	Enlist the methods for detecting peaks and valleys. Describe any methods for detecting peaks and valleys with an example	3
(b)	Explain the term Delay Equalization in brief with suitable examples.	3

6. Attempt any *one* part of the following: **10\*1 = 10**

Q. No	Questions	CO
(a)	Discuss Burton's FDNR Techniques with suitable examples.	4
(b)	Briefly explain the term Ladder design. Illustrate with an example	4

7. Attempt any *one* part of the following: **10\*1 = 10**

Q. No	Questions	CO
(a)	Provide the brief Notes on: (I) C-Filters (II) Voltage limiting	5
(b)	Explain Notch and AP transfer functions with an example.	5