

B. TECH.
(SEM-III) THEORY EXAMINATION 2018-19
DIGITAL LOGIC DESIGN

Time: 3 Hours**Total Marks: 70****Note: 1.** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief.****2 x 7 = 14**

- a. Define Digital System?
- b. Write the definition of the Duality Theorem?
- c. Define Rise Time?
- d. What is the binary number system?
- e. State the De Morgan's Theorem?
- f. What are the applications of Flip-Flops?
- g. What is the difference between Synchronous and Asynchronous Counters?

SECTION B**2. Attempt any three of the following:****7 x 3 = 21**

- a. What are prime implicant and essential prime implicant? simplify the Boolean function using K-Map and identify them
 $f(a,b,c,d) = \sum m(0,1,2,5,6,7,8,9,10,13,14,15)$
- b. Design a combinational logic circuit to check for even parity of three bits.
- c. Using Quine McCluskey method & PI reduction table, determine the minimal SOP expression for the following using decimal notation
 $f = \sum m(1,4,7,9,12,14) + \sum d(2,13)$
- d. Write the compressed truth table for a 4 to 2 line priority encoder with a valid output and simplify the same using K-Map. Design the logic circuit for the same.
- e. With the aid of block diagram clearly distinguish between a decoder and encoder.

SECTION C**3. Attempt any one part of the following:****7 x 1 = 7**

- (a) Add and multiply the following numbers in the given base without converting to decimal: (i) $(123)_4$ and $(321)_4$ (ii) $(567)_8$ and $(234)_8$.
- (b) Convert the decimal number 246.8 to base 3, base 5 and base 7.

4. Attempt any one part of the following:**7 x 1 = 7**

- (a) Explain about ROM and PROM.
- (b) Draw the basic circuit of the RTL NOR gate. Explain the operation.

5. Attempt any one part of the following:**7 x 1 = 7**

- (a) With the help of logic diagram, explain the 4 bit universal shift register using D flip-flops and 4:1 MUX.
- (b) Write the truth table of the SR, JK, D & T flip-flops.

6. Attempt any one part of the following:**7 x 1 = 7**

- (a) Simplify following logic function and realize using NOR gates.
 $f(w,x,y,z) = \pi M(1,2,3,7,10,11) + d(0,15)$
 $f(w,x,y,z) = \pi M(3,4,5,6,7,10,11,15)$
- (b) Draw the basic circuit for the DTL NAND gate. Explain the operation.

7. Attempt any one part of the following:**7 x 1 = 7**

- (a) What is asynchronous counter? How would you design asynchronous counter?
- (b) Design a BCD counter with JK flip flops.