

B. TECH
(SEM-III) THEORY EXAMINATION 2022-23
DIGITAL LOGIC DESIGN

Time: 3 Hours**Total Marks: 70****Note:** Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt all questions in brief.**2 x 7 = 14**

- (a) Draw a full adder using two half adders
- (b) What is Modulus of a counter?
- (c) What is the difference between Synchronous and Asynchronous sequential circuits
- (d) What do you mean by race around condition in JK Flip Flop?
- (e) What is the difference between Multiplexer and Encoder
- (f) Write the canonical form of $Y = (A+D)(B+C)(C+D)$
- (g) Convert $(554.423)_{10}$ to an Hexadecimal number

SECTION B

2. Attempt any three of the following;**7 x 3 = 21**

- (a) Draw the basic circuit of the RTL NOR gate. Explain the operation.
- (b) Implement the function $F = \sum m(0,1,3,4,7,8,9,11,14,15)$ using 8:1 mux.
- (c) Draw and explain 2-bit magnitude comparator.
- (d) Using Quine McCluskey method, determine the minimal SOP expression for the following using decimal notation $f = \sum m(1,4,7,9,12,14) + \sum d(2,13)$
- (e) Draw and explain the SISO, PISO right shift register.

SECTION C

3. Attempt any one part of the following:**7 x 1 = 7**

- (a) Write the compressed truth table for a 4 to 2 line priority encoder with a valid output and simplify the same using K-Map. Design the logic circuit for the same.
- (b) Design a combinational logic circuit to check for odd parity of three bits.

4. Attempt any one part of the following:**7 x 1 = 7**

- (a) What is race around condition? How can it be avoided?
- (b) Convert the decimal number 246.8 to base 3, base 5 and base 7.

5. Attempt any *one* part of the following:

7 x 1 = 7

- (a) Design a BCD counter with D flip flops.
- (b) Draw JK flip flop & write its Excitation table and characteristic equation.

6. Attempt any *one* part of the following:

7 x 1 = 7

- (a) Design a 3-bit Up/Down ripple counter.
- (b) An asynchronous sequential logic circuit is described by the following excitation and output function

$$y = X_1X_2 + (X_1 + X_2)Y$$


$$Z = y$$

Draw the logic diagram of the circuit, Also derive the transition table and output map.

7. Attempt any *one* part of the following:

7 x 1 = 7

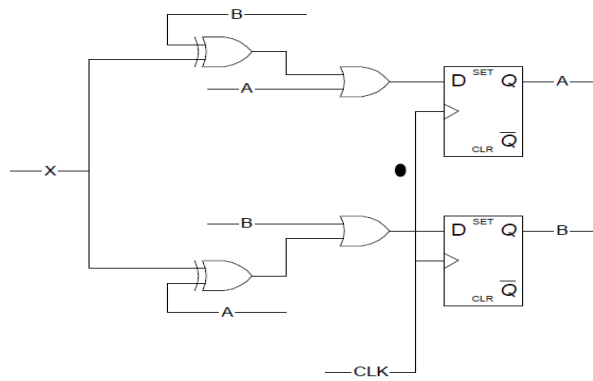- (a) Derive the state table and state diagram of the synchronous sequential circuit shown below (X is an input to the circuit). Explain the circuit function.



- (b) Simplify following logic function using K-Map and realize using NOR gates.

$$f(w,x,y,z) = \pi M(1,2,3,7,10,11) + d(0,15)$$