

Paper Id: 130317

Roll No: 

--	--	--	--	--	--	--	--	--	--	--	--

**B.TECH**  
**(SEM-III) THEORY EXAMINATION 2019-20**  
**SWITCHING THEORY & LOGIC DESIGN**

**Time: 3 Hours****Total Marks: 100****Note:** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A**

- 1. Attempt all questions in brief. 2 x 10 = 20**
- Name the two forms of Boolean expression?
  - What is Half-Adder?
  - What are Minterm and Maxterm?
  - What is a Multiplexer?
  - Write down the Characteristics of Digital ICs?
  - Define fall time?
  - For the hamming code 1001101001 received at the receiver end, correct this code for error if any.
  - Convert the hexadecimal number (BE86) in binary and convert it from binary to octal.
  - What is synchronous sequential circuit?
  - Distinguish between weighted binary codes and unweighted binary code.

**SECTION B**

- 2. Attempt any three of the following: 10x3=30**
- Design MOD 11 synchronous counter using T flip flop.
  - Implement 4 bit magnitude comparator.
  - Design a BCD counter with JK flip flops.
  - Draw truth table and circuit of JK flip flop using NAND gates.
  - A 6:64 decoder is to be implemented using 3:8 decoders only. Show the block diagram of 6:64 decoder.

**SECTION C**

- 3. Attempt any one part of the following: 10x1=10**
- With the help of logic diagram, explain working of Master slave JK Flip-Flop along with waveforms. Explain race around condition. How is it eliminated?
  - Write the truth table of the SR, D & T flip-flops.
- 4. Attempt any one part of the following: 10x1=10**
- Construct Moore and Mealy state diagram that will detect input sequence 10110, when input pattern is detected, z is asserted high. Give state diagram for each state.
  - Solve the following Boolean functions by using K-Map : F  
 $(w,x,y,z) = \Sigma(0,1,4,5,6,8,9,10,12,13,14)$
- 5. Attempt any one part of the following: 10x1=10**
- Write a short note on Encoders. Discuss their applications. Design an 8- Input Priority Encoder using basic gates.
  - What is number system? Explain 1's complement and 2's complement with example.
- 6. Attempt any one part of the following: 10x1=10**
- Simplify following logic function and realize using NOR gates.  
 $f(w,x,y,z) = \pi M(1,2,3,7,10,11) + d(0,15)$   
 $f(w,x,y,z) = \pi M(3,4,5,6,7,10,11,15)$
  - What is the function of binary multiplier? Explain.
- 7. Attempt any one part of the following: 10x1=10**
- Explain about ROM and PROM.
  - Draw the basic circuit of the RTL NOR gate. Explain the operation.